

HW2 + Simulations

FPGA & ASIC

Ali Naghiloo 40010093

FPGA & ASIC

Dr. Hosseini-Nejad

1403/02/22

Designed By:

AN



1928
K. N. Toosi
University of Technology
Faculty of Electrical Engineering

Top-Module Code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity convolution is
    generic(conv_width : integer := 8);
    Port ( CLK : in STD_LOGIC;
          input_a : in STD_LOGIC_VECTOR (conv_width-1 downto 0);
          input_x : in STD_LOGIC_VECTOR (conv_width-1 downto 0);
          Y : out STD_LOGIC_VECTOR (19 downto 0));
end convolution;

architecture Behavioral of convolution is
    signal W1,W2 : STD_LOGIC_VECTOR (conv_width-1 downto 0);
    signal W3 : STD_LOGIC_VECTOR (15 downto 0);
    signal W4,W5 : STD_LOGIC_VECTOR (19 downto 0);
    signal W6 : STD_LOGIC;
begin

inA: entity work.reg generic map(8)port map(CLK,'0','1',input_a,W1);
inX: entity work.reg generic map(8)port map(CLK,'0','1',input_x,W2);
multiplier: entity work.multiplier generic map(8)port map(W1,W2,W3);
adder: entity work.adder generic map(16,20)port map(W3,W4,W5);
adder_reg: entity work.reg generic map(20)port map(CLK,W6,'1',W5,W4);
counter: entity work.counter generic map(9) port map(RCO=>W6,CLK=>clk);
output_reg: entity work.reg generic map(20)port map(CLK,'0',W6,W5,Y);
end Behavioral;

```

----- TB -----

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity convolution_TB is
end convolution_TB;

architecture behavior of convolution_TB is
    constant conv_width : integer := 8;
    signal CLK : STD_LOGIC := '0';
    signal input_a : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal input_x : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal Y : STD_LOGIC_VECTOR (19 downto 0);

    component convolution
        generic(conv_width : integer := 8);
        port(
            CLK : in STD_LOGIC;
            input_a : in STD_LOGIC_VECTOR (conv_width-1 downto 0);
            input_x : in STD_LOGIC_VECTOR (conv_width-1 downto 0);
            Y : out STD_LOGIC_VECTOR (19 downto 0)
        );
    end component;

    -- Clock period definitions
    constant CLK_period : time := 90ns;

begin

```

```

    uut: convolution generic map(conv_width) port map (
        CLK => CLK,
        input_a => input_a,
        input_x => input_x,
        Y => Y
    );

CLK <= not CLK after CLK_period/2;

-- Stimulus process
stim_proc: process
begin

    input_a <= b"0000_1011"; input_x <= b"0001_1011";
    wait for CLK_period*2;
    input_a <= b"0001_1011"; input_x <= b"1001_1111";
    wait for CLK_period*3;
    input_a <= b"1001_1000"; input_x <= b"1001_1001";
    wait for CLK_period*4;
    input_a <= b"0000_0000"; input_x <= b"1001_0010";
    wait for CLK_period*2;
    input_a <= b"1001_1011"; input_x <= b"1001_1100";
    wait for CLK_period*5;
    input_a <= b"1001_1000"; input_x <= b"1000_1001";
    wait;
end process;


end;
```

Utilization-synth & synthesis report is as follows:


```
Start RTL Component Statistics
-----
Detailed RTL Component Info :
+---Adders :
      2 Input    20 Bit      Adders := 1
+---Registers :
              20 Bit    Registers := 2
              8 Bit     Registers := 2
```

Site Type	Used	Fixed	Prohibited	Available	Util%
Bonded IOB	20	0	0	100	20.00
PHY_CONTROL	0	0	0	2	0.00
PHASER_REF	0	0	0	2	0.00
OUT_FIFO	0	0	0	8	0.00
IN_FIFO	0	0	0	8	0.00
IDELAYCTRL	0	0	0	2	0.00
IBUFDS	0	0	0	96	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	0	8	0.00
PHASER_IN/PHASER_IN_PHY	0	0	0	8	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	0	100	0.00
ILOGIC	0	0	0	100	0.00
LOGIC	0	0	0	100	0.00


RTL Schematic is as follows:

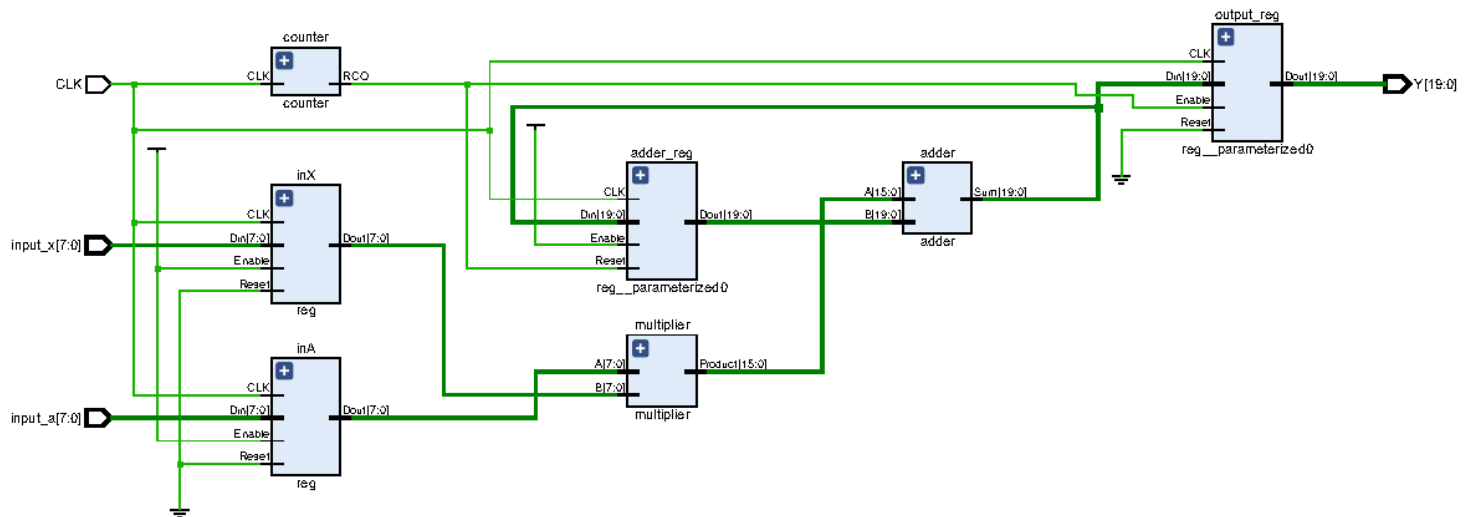

LUT Schematic:

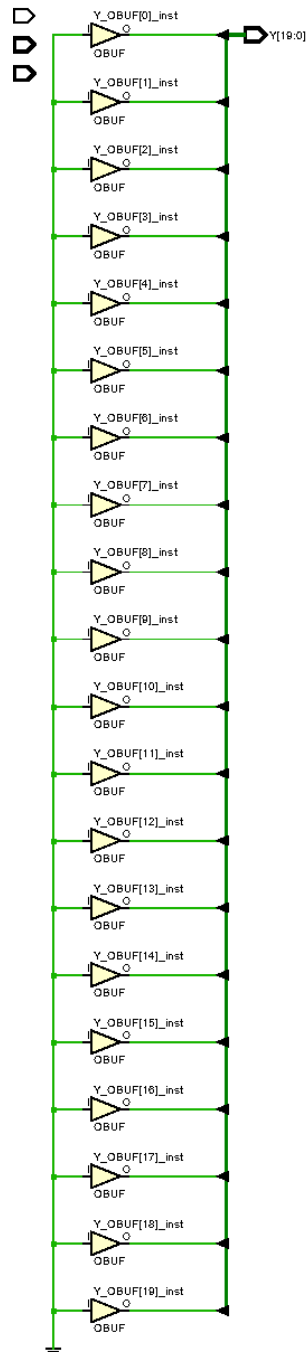

Waveform

 

Sub-Modules Code:**REG**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity reg is
    generic(SR_width : integer := 8);
    Port ( CLK : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Enable : in STD_LOGIC;
          Din : in STD_LOGIC_VECTOR (SR_width-1 downto 0);
          Dout : out STD_LOGIC_VECTOR (SR_width-1 downto 0));
end reg;

architecture Behavioral of reg is
    signal temp_dout : STD_LOGIC_VECTOR (SR_width-1 downto 0) :=(others => '0');
begin

    process(CLK)
    begin

        if (clk'event and clk='1') then

            if (reset='1') then
                temp_dout <= (others => '0');
            elsif (enable='1') then
                temp_dout <= din;
            end if;

        end if;
    end process;
    dout <= temp_dout;
end Behavioral;

```

----- TB -----

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity reg_tb is
end reg_tb;

architecture behavior of reg_tb is
    -- Component Declaration for the Unit Under Test (UUT)
    component reg
        generic(SR_width : integer := 8);
        port(
            CLK : in STD_LOGIC;
            Reset : in STD_LOGIC;
            Enable : in STD_LOGIC;
            Din : in STD_LOGIC_VECTOR (SR_width-1 downto 0);
            Dout : out STD_LOGIC_VECTOR (SR_width-1 downto 0)
        );
    end component;

    --Inputs
    constant SR_width : integer := 8;
    signal CLK : STD_LOGIC := '0';
    signal Reset : STD_LOGIC := '0';
    signal Enable : STD_LOGIC := '0';
    signal Din : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');

    --Outputs
    signal Dout : STD_LOGIC_VECTOR (7 downto 0);

```

```

-- Clock period definitions
constant CLK_period : time := 50 ns;

begin

    -- Instantiate the Unit Under Test (UUT)
    uut: reg generic map (SR_width => SR_width)
        port map (
            CLK => CLK,
            Reset => Reset,
            Enable => Enable,
            Din => Din,
            Dout => Dout
        );

    -- Clock process definitions
    CLK_process : process
    begin
        CLK <= '0';
        wait for CLK_period/2;
        CLK <= '1';
        wait for CLK_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 500 ns.
        Reset <= '1';
        -- insert stimulus here
        wait for CLK_period*6.5;
        Enable <= '1'; Din <= "10011011";
        wait for CLK_period*4;
        Din <= "10000000";
        wait for CLK_period*8;
        Din <= "10000010";
        wait for CLK_period*7;
        Enable <= '0';
        wait for CLK_period*10;
        Din <= "00000000";
        wait for CLK_period*5;
        Din <= "00000001";
        wait;
    end process;

end;
```


Adder:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.std_logic_unsigned.ALL;

entity adder is
    generic(adder_width1 : integer :=16;
            adder_width2 : integer :=20);
    Port ( A : in STD_LOGIC_VECTOR (adder_width1-1 downto 0);
          B : in STD_LOGIC_VECTOR (adder_width2-1 downto 0);
          Sum : out STD_LOGIC_VECTOR (adder_width2-1 downto 0));
end adder;

```

```

architecture Behavioral of adder is

```

```

begin

```

```

Sum <= A + B;

```

```

end Behavioral;

```

```

----- TB -----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity adder_TB is

```

```

-- Port ( );

```

```

end adder_TB;

```

```

architecture Behavioral of adder_TB is

```

```

    constant adder_width1 : integer :=16;

```

```

    constant adder_width2 : integer :=20;

```

```

    signal A : STD_LOGIC_VECTOR (adder_width1-1 downto 0);

```

```

    signal B : STD_LOGIC_VECTOR (adder_width2-1 downto 0);

```

```

    signal Sum : STD_LOGIC_VECTOR (adder_width2-1 downto 0);

```

```

    component adder is

```

```

        generic(adder_width1 : integer :=16;

```

```

                adder_width2 : integer :=20);

```

```

        Port ( A : in STD_LOGIC_VECTOR (adder_width1-1 downto 0);

```

```

              B : in STD_LOGIC_VECTOR (adder_width2-1 downto 0);

```

```

              Sum : out STD_LOGIC_VECTOR (adder_width2-1 downto 0));

```

```

    end component;

```

```

begin

```

```

DUT1: adder generic map(adder_width1,adder_width2) port map(A=>A,B=>B,Sum=>sum);

```

```

A <= b"0000_1011",b"1001_1111" after 10ns,b"0001_1101" after 20ns;

```

```

B <= b"0010_1011",b"0001_1001" after 5ns,b"0001_0001" after 18ns,b"1001_1101" after 25ns;

```

```

end Behavioral;

```

Multiplier:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.std_logic_unsigned.ALL;

entity multiplier is
    generic(mult_width : integer :=8);
    Port ( A : in STD_LOGIC_VECTOR (mult_width-1 downto 0);
          B : in STD_LOGIC_VECTOR (mult_width-1 downto 0);
          Product : out STD_LOGIC_VECTOR (2*mult_width-1 downto 0));
end multiplier;

architecture Behavioral of multiplier is
    signal extra : std_logic_vector(2*mult_width-1 downto 0);
begin

    product <= conv_std_logic_vector(conv_integer(A * B),2*mult_width);

end Behavioral;
----- TB -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity multiplier_TB is
    -- Port ( );
end multiplier_TB;

architecture Behavioral of multiplier_TB is

    constant mult_width : integer :=8;
    signal A : STD_LOGIC_VECTOR (mult_width-1 downto 0);
    signal B : STD_LOGIC_VECTOR (mult_width-1 downto 0);
    signal Product : STD_LOGIC_VECTOR (2*mult_width-1 downto 0);

    component multiplier is
        generic(mult_width : integer :=8);
        Port ( A : in STD_LOGIC_VECTOR (mult_width-1 downto 0);
              B : in STD_LOGIC_VECTOR (mult_width-1 downto 0);
              Product : out STD_LOGIC_VECTOR (2*mult_width-1 downto 0));
    end component;

begin

    DUT1: multiplier generic map(mult_width=>mult_width) port map(A=>A,B=>B,Product=>Product);

    A <= b"0000_1011",b"0000_1111" after 10ns,b"0001_1101" after 20ns;
    B <= b"0000_1011",b"0000_1001" after 5ns,b"0000_0001" after 18ns,b"0000_0001" after 25ns;

end Behavioral;

```

Counter:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.std_logic_unsigned.ALL;

entity counter is
    generic(interval : integer :=10);
    Port ( CLK : in STD_LOGIC;
          RCO : out STD_LOGIC);
end counter;

architecture Behavioral of counter is
    signal count : integer range 0 to interval-1 :=0;
    signal temp_RCO : std_logic :='0';
begin
    process(clk)
    begin

        if (clk'event and clk='1') then

            count <= count + 1;
            if (count = interval) then
                count <= 0;
            end if;

        end if;
    end process;

    temp_RCO <= '1' when count=interval else '0';
    RCO <= temp_RCO;

end Behavioral;

```

----- TB -----

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity counter_TB is
    -- Port ( );
end counter_TB;

architecture Behavioral of counter_TB is
    signal CLK : STD_LOGIC :='0';
    signal RCO : STD_LOGIC;
    component counter is
        generic(interval : integer);
        Port ( CLK : in STD_LOGIC;
              RCO : out STD_LOGIC);
    end component;
    constant period : time := 90ns;
begin

    clk <= not clk after (period/2);
    DUT1: counter generic map(10) port map(CLK=>CLK,RCO=>RCO);

end Behavioral;

```