

# HW1 + Simulations

## FPGA & ASIC

Ali Naghiloo 40010093

FPGA & ASIC

Dr. Hosseini-Nejad

1403/02/16

Designed By:

AE



1928  
K. N. Toosi  
University of Technology  
Faculty of Electrical Engineering

**Q1) Code:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity parity_checker is
    Port ( input : in STD_LOGIC_VECTOR (7 downto 0);
          even_parity : buffer STD_LOGIC;
          output : out STD_LOGIC_VECTOR (8 downto 0));
end parity_checker;

architecture DataFlow of parity_checker is
    -----
    function even_parity_maker (a1 : in std_logic_vector)
    return std_logic
    is
        variable b1 : STD_LOGIC := '0';

        begin
        loop1: for i in a1'range loop
            b1 := a1(i) xor b1;
        end loop;

        return b1;
    end function;
    -----

    signal preout1 : std_logic_vector(8 downto 0);
    signal preout2 : std_logic_vector(8 downto 0);

    begin
    preout1 <= ('0' & input + 47);
    preout2 <= ('0' & input - 37);

    even_parity <= even_parity_maker(input);
    with even_parity select
        output    <= ('0' & preout1(8 downto 1)) when '0',
                    (preout2(7 downto 0) & '0') when others;

end DataFlow;

```

```

----- TB -----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Parity_checker_TB is
    -- Port ( );
end Parity_checker_TB;

architecture DataFlow of Parity_checker_TB is
    signal input : STD_LOGIC_VECTOR (7 downto 0);
    signal even_parity : STD_LOGIC;
    signal output : STD_LOGIC_VECTOR (8 downto 0);
    component Parity_checker
        Port ( input : in STD_LOGIC_VECTOR (7 downto 0);
              even_parity : buffer STD_LOGIC;
              output : out STD_LOGIC_VECTOR (8 downto 0));
    end component;
    begin
    UUT1: Parity_checker port map(input,even_parity,output);

    input <= b"1100_1010",
            b"1100_1011" after 200 ns,
            b"1010_1010" after 400 ns,
            b"1110_1010" after 600 ns;

end DataFlow;

```

Utilization-synth & synthesis report is as follows:

1. Slice Logic

---

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	14	0	0	3750	0.37
LUT as Logic	14	0	0	3750	0.37
LUT as Memory	0	0	0	2400	0.00
Slice Registers	0	0	0	7500	0.00
Register as Flip Flop	0	0	0	7500	0.00
Register as Latch	0	0	0	7500	0.00
F7 Muxes	0	0	0	4000	0.00
F8 Muxes	0	0	0	2000	0.00

#### Detailed RTL Component Info :

----Adders :

2 Input 9 Bit Adders := 1

2 Input 8 Bit Adders := 1

----XORs :

8 Input 1 Bit XORs := 1

----Muxes :

2 Input 9 Bit Muxes := 1

#### Finished RTL Component Statistics

#### Start Part Resource Summary

#### Part Resources:

DSPs: 10 (col length:20)

BRAMs: 10 (col length: RAMB18 20 RAMB36 10)

#### 7. Primitives

---


Ref Name	Used	Functional Category
OBUF	10	IO
LUT6	10	LUT
IBUF	8	IO
LUT5	4	LUT
LUT4	3	LUT

#### 4. IO and GT Specific


---

Site Type	Used	Fixed	Prohibited	Available	Util%
Bonded IOB	18	0	0	100	18.00
PHY_CONTROL	0	0	0	2	0.00
PHASER_REF	0	0	0	2	0.00
OUT_FIFO	0	0	0	8	0.00
IN_FIFO	0	0	0	8	0.00
IDELAYCTRL	0	0	0	2	0.00
IBUFDS	0	0	0	96	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	0	8	0.00
PHASER_IN/PHASER_IN_PHY	0	0	0	8	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	0	100	0.00
ILOGIC	0	0	0	100	0.00
OLOGIC	0	0	0	100	0.00

RTL Schematic is as follows:

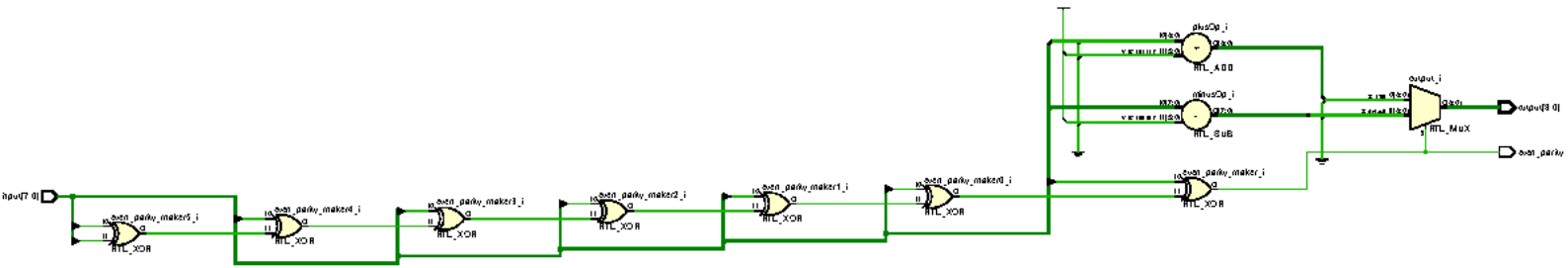

LUT Schematic:

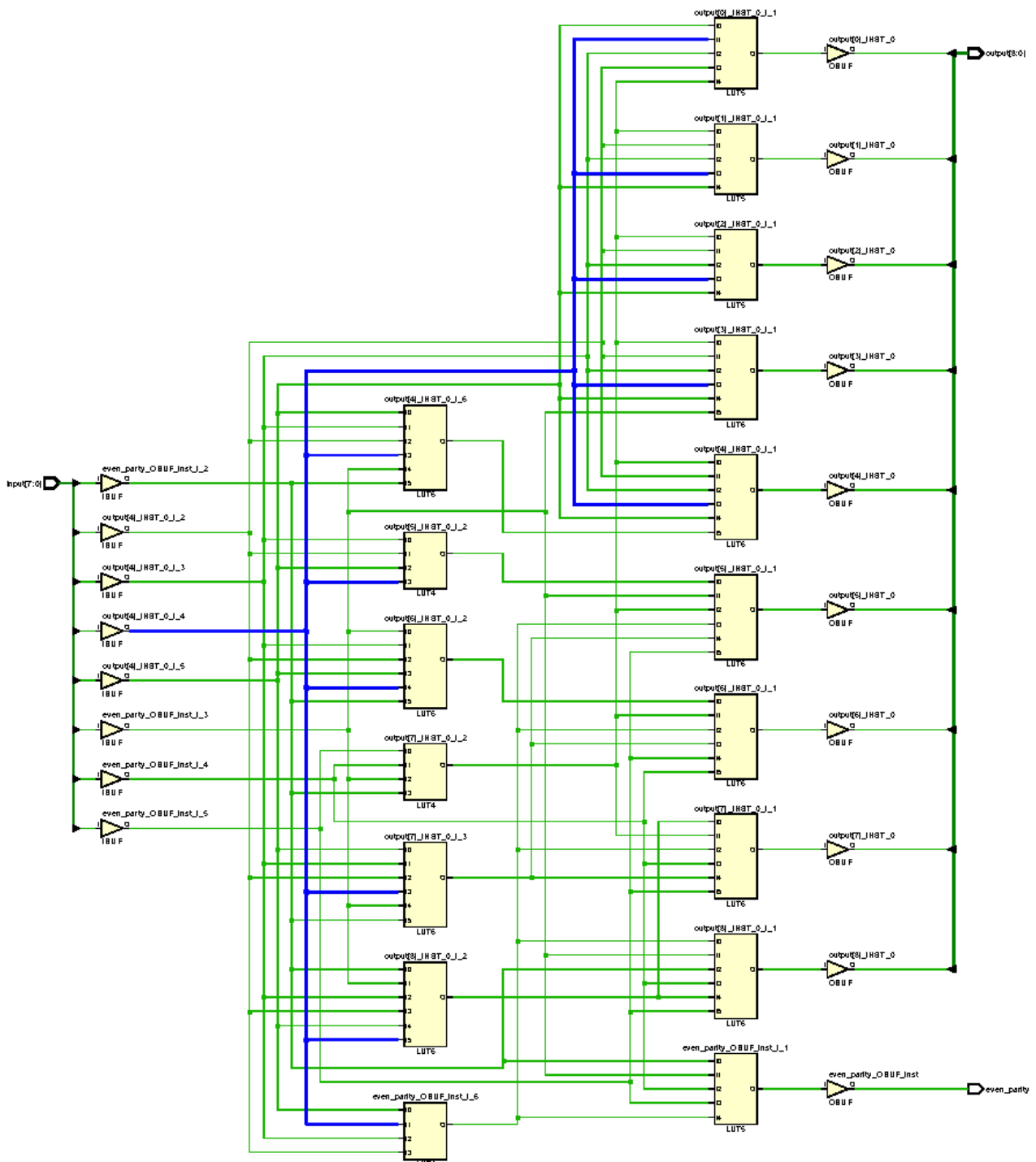

## Waveform

## Binary:

Name	Value	0.000 ns	200.000 ns	400.000 ns	600.000 ns	800.000 ns
>  input[7:0]	11101010	11001010	11001011	10101010	11101010	
even_parity	1					
>  output[8:0]	110001010	001111100	101001100	001101100	110001010	

## Decimal:

Name	Value	0.000 ns	200.000 ns	400.000 ns	600.000 ns	800.000 ns
>  input[7:0]	234	202	203	170	234	
even_parity	1					
>  output[8:0]	394	124	332	108	394	

For example, we check the first one:

If "input" is  $[11001010]_2 = [202]_{10}$  then "even\_parity" should be "0" because the counts of "1" in "11001010" is four ! and "output" should be  $(202+47)/2 = 124.5$  . ✓

**Q2] Code:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity stopwatch is
    Port ( CLK : in STD_LOGIC;
          Async_Reset : in STD_LOGIC;
          Start : in STD_LOGIC;
          CS : BUFFER INTEGER RANGE 0 TO 100;
          S : BUFFER INTEGER RANGE 0 TO 60;
          M : BUFFER INTEGER RANGE 0 TO 60);
end entity;

architecture Behavioral of stopwatch is
begin

    process(CLK,Async_Reset)
        variable count_internal : integer range 0 to 2 :=0;
    begin

        if (Async_reset = '1') then

            CS <= 0;
            S <= 0;
            M <= 0;

        elsif (clk'event and clk = '1') then

            if (start = '1') then
                count_internal := count_internal+1;
                if(count_internal=2) then
                    count_internal := 1;
                    CS <= CS+1;
                    if(CS = 99) then
                        CS <= 0;
                        S <= S+1;
                        if(S = 59) then
                            S <= 0;
                            M <= M+1;
                            if(M = 59) then
                                M <= 0;
                                report("1 hour !")
                                severity(Failure);
                            end if;
                        end if;
                    end if;
                end if;
            end if;
        end if;
    end process;
end architecture;

```

```

----- TB -----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity stopwatch_TB is
    -- Port ( );
end stopwatch_TB;

architecture Behavioral of stopwatch_TB is
    signal CLK : STD_LOGIC:='0';
    signal Async_Reset : STD_LOGIC;
    signal Start : STD_LOGIC;
    signal CS : INTEGER RANGE 0 TO 100;
    signal S : INTEGER RANGE 0 TO 60;
    signal M : INTEGER RANGE 0 TO 60;
    component stopwatch
        Port ( CLK : in STD_LOGIC;
              Async_Reset : in STD_LOGIC;
              Start : in STD_LOGIC;
              CS : BUFFER INTEGER RANGE 0 TO 100;
              S : BUFFER INTEGER RANGE 0 TO 60;
              M : BUFFER INTEGER RANGE 0 TO 60);
    end component;
    constant period : time :=10 ms;

```

```

begin
DUT: stopwatch port map(CLK, Async_Reset, Start, CS, S, M);
CLK <= not CLK after (period/2);
Async_Reset <= '1', '0' after (2*period);
stimulus: process
begin
Start<= '1';
wait for (2*period);
Start<= '0';
wait for (2.25*period);
Start<= '1';
wait;
end process;
end Behavioral;

```

Utilization-synth & synthesis report is as follows:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	32	0	0	3750	0.85
LUT as Logic	32	0	0	3750	0.85
LUT as Memory	0	0	0	2400	0.00
Slice Registers	36	0	0	7500	0.48
Register as Flip Flop	36	0	0	7500	0.48
Register as Latch	0	0	0	7500	0.00
F7 Muxes	0	0	0	4000	0.00
F8 Muxes	0	0	0	2000	0.00

Total	Clock Enable	Synchronous	Asynchronous
0	-	-	-
0	-	-	Set
0	-	-	Reset
0	-	Set	-
0	-	Reset	-
0	Yes	-	-
0	Yes	-	Set
19	Yes	-	Reset
1	Yes	Set	-
16	Yes	Reset	-

Site Type	Used	Fixed	Prohibited	Available	Util%
Bonded IOB	22	0	0	100	22.00
PHY_CONTROL	0	0	0	2	0.00
PHASER_REF	0	0	0	2	0.00
OUT_FIFO	0	0	0	8	0.00
IN_FIFO	0	0	0	8	0.00
IDELAYCTRL	0	0	0	2	0.00
IBUFDS	0	0	0	96	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	0	8	0.00
PHASER_IN/PHASER_IN_PHY	0	0	0	8	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	0	100	0.00
ILOGIC	0	0	0	100	0.00
OLOGIC	0	0	0	100	0.00



Site Type	Used	Fixed	Prohibited	Available	Util%
BUFGCTRL	1	0	0	16	6.25
BUFIO	0	0	0	8	0.00
MMCME2_ADV	0	0	0	2	0.00
PLLE2_ADV	0	0	0	2	0.00
BUFMRCE	0	0	0	4	0.00
BUFHCE	0	0	0	24	0.00
BUFR	0	0	0	8	0.00

#### Detailed RTL Component Info :

##### +---Adders :

2 Input 17 Bit Adders := 1

2 Input 7 Bit Adders := 1

2 Input 6 Bit Adders := 2

##### +---Registers :

7 Bit Registers := 1


6 Bit Registers := 2

##### +---Muxes :


2 Input 6 Bit Muxes := 2

2 Input 1 Bit Muxes := 3

RTL Schematic is as follows:



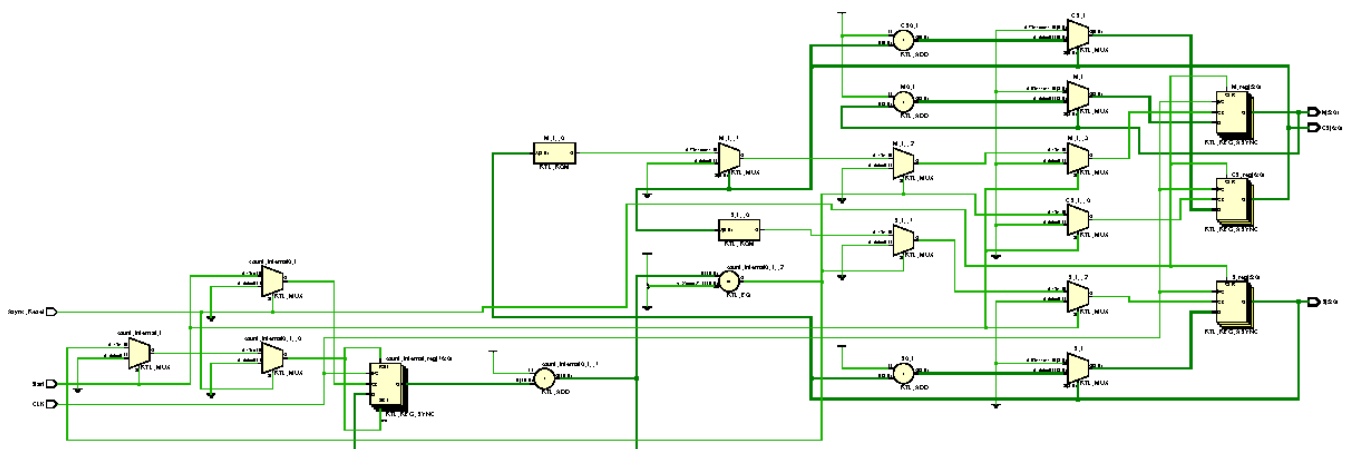


LUT Schematic:

 



## Waveforms

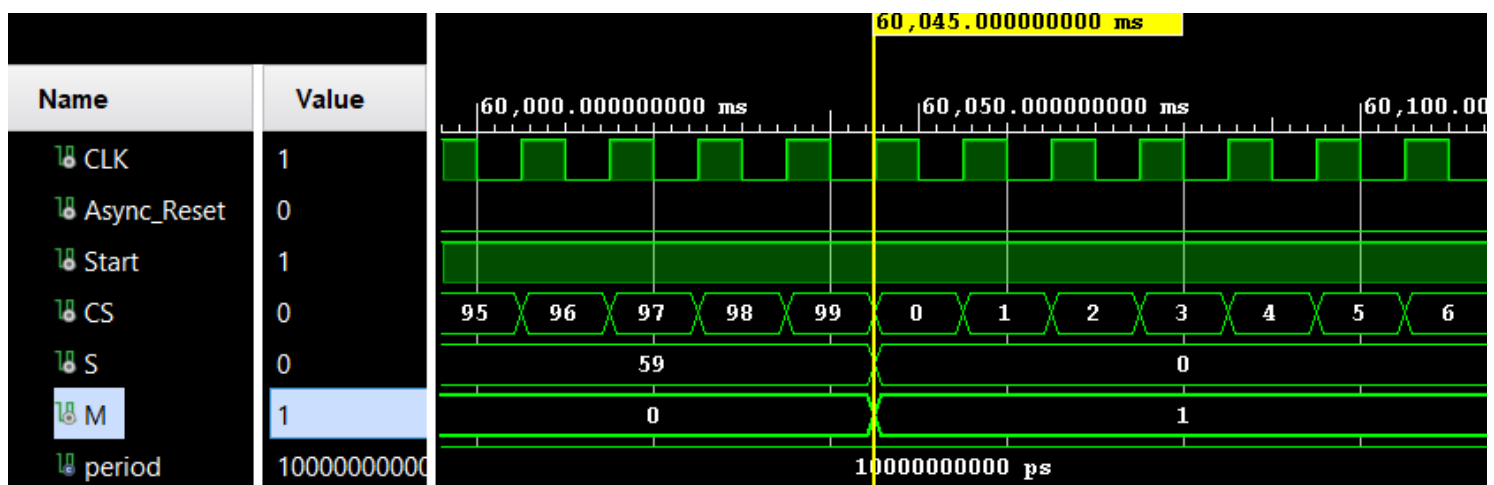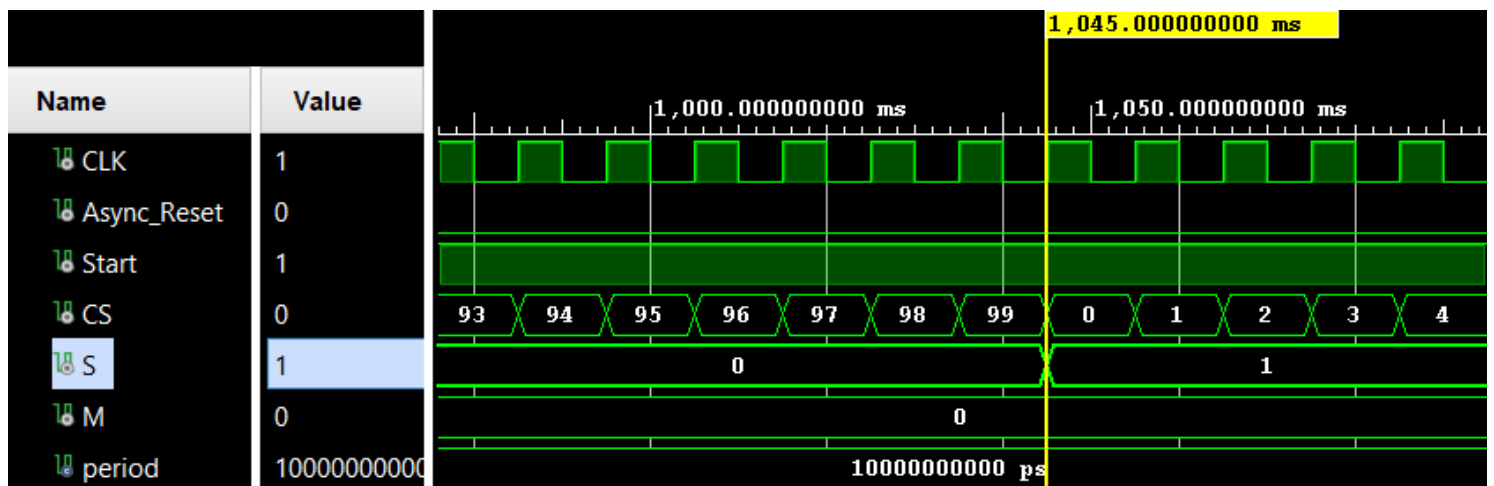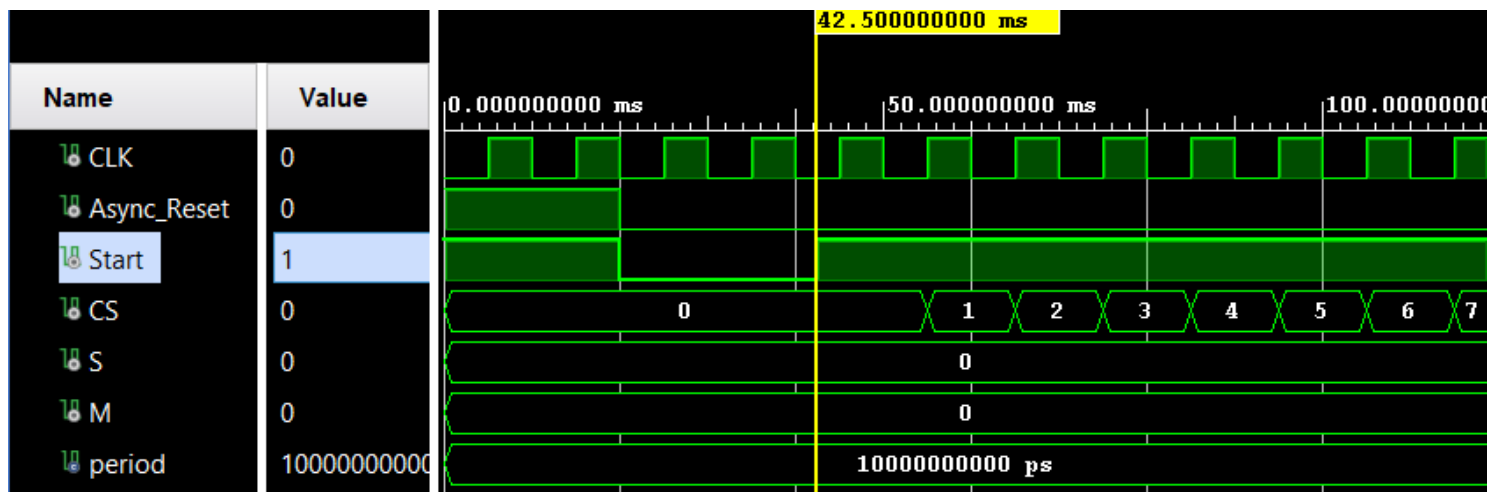

**Q3] Code:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity frequency_divider is
    Port ( clk : in STD_LOGIC;
          duty_cycle : in STD_LOGIC_VECTOR (3 downto 0);
          clk_out : out STD_LOGIC);
end entity;

architecture Behavioral of frequency_divider is
    signal count : integer range 0 to 99 := 0;
begin
    process(clk)
    begin
        if (clk'event and clk='1') then
            if count = 99 then
                count <= 0;
            else
                count <= count + 1;
            end if;
            if (count < 10*(conv_integer(duty_cycle))) then
                clk_out <= '1';
            else
                clk_out <= '0';
            end if;
        end if;
    end process;
end architecture;

```

```

----- TB -----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity frequency_divider_TB is
--    Port ( );
end frequency_divider_TB;

architecture Behavioral of frequency_divider_TB is
    signal clk : STD_LOGIC := '0';
    signal duty_cycle : STD_LOGIC_VECTOR (3 downto 0);
    signal clk_out : STD_LOGIC;
    component frequency_divider
        Port ( clk : in STD_LOGIC;
              duty_cycle : in STD_LOGIC_VECTOR (3 downto 0);
              clk_out : out STD_LOGIC);
    end component;
    constant period : time := 125 ns;
    begin
        DUT: frequency_divider port map(CLK,duty_cycle,clk_out);
        CLK <= not CLK after (period/2);

        stimulus: process
        begin
            duty_cycle <= x"1";
            wait for (400*period);
            duty_cycle <= x"0";
            wait for (400*period);
            duty_cycle <= x"9";
            wait for (400*period);
            duty_cycle <= x"5";
            wait for (400*period);
            duty_cycle <= x"3";
            wait;
        end process;
    end Behavioral;

```

Utilization-synth & synthesis report is as follows:

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	11	0	0	3750	0.29
LUT as Logic	11	0	0	3750	0.29
LUT as Memory	0	0	0	2400	0.00
Slice Registers	8	0	0	7500	0.11
Register as Flip Flop	8	0	0	7500	0.11
Register as Latch	0	0	0	7500	0.00
F7 Muxes	0	0	0	4000	0.00
F8 Muxes	0	0	0	2000	0.00

Resource	Estimation	Available	Utilization %
LUT	11	3750	0.29
FF	8	7500	0.11
IO	6	100	6.00
BUFG	1	16	6.25

Detailed RTL Component Info :

+---Adders :


2 Input 7 Bit Adders := 1

+---Registers :


7 Bit Registers := 1

1 Bit Registers := 1


RTL Schematic is as follows:

 


LUT Schematic:

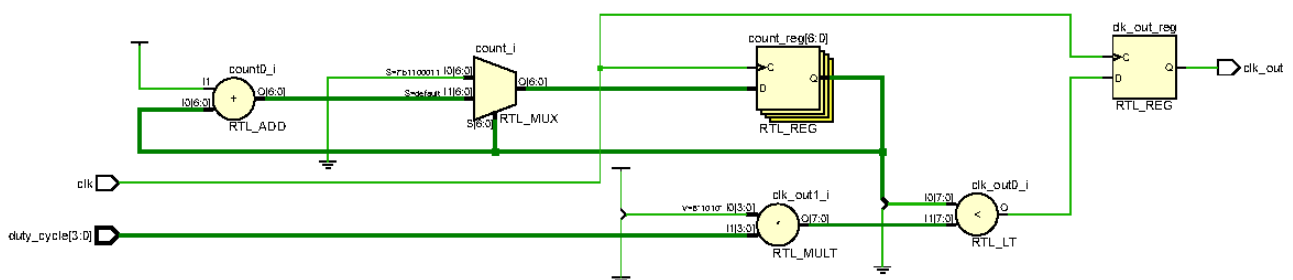

## Waveforms

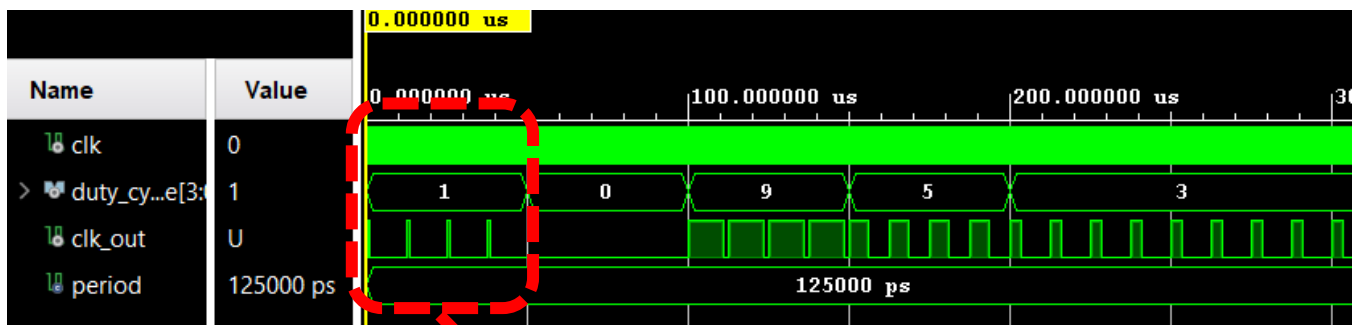

ZOOM

 

## Product:

**i** The default part and product family for the new project:  
 Default Part: xc7s6cpga196-2  
 Family: Spartan-7  
 Package: cpga196  
 Speed Grade: -2